

Myrelia I. Villa

- Code

```
// state encoding and state variable
enum logic[3:0]{
    RX_IDLE = 4'b0000,
    RX_START_BIT = 4'b0001,
    RX_DATA_BIT0 = 4'b0010,
    RX_DATA_BIT1 = 4'b0011,
    RX_DATA_BIT2 = 4'b0100,
    RX_DATA_BIT3 = 4'b0101,
    RX_DATA_BIT4 = 4'b0110,
    RX_DATA_BIT5 = 4'b0111,
    RX_DATA_BIT6 = 4'b1000,
    RX_DATA_BIT7 = 4'b1001,
    RX_STOP_BIT = 4'b1010} state;
// FSM with single always block for next state,
// present state flipflop and output logic
always_ff@(posedge clk) begin
    if(!rstn) begin
        done <= 0;
        count <= 0;
        dout <= 0;
        state <= RX_IDLE;
    end
    else begin
        case(state)
            RX_IDLE: begin
                done <= 0;
                count <= 0;
                dout <= 0;
                // Wait for rx = 0 indicating start bit
                if(rx == 0) state <= RX_START_BIT;
                else state <= RX_IDLE;
            end
            RX_START_BIT: begin
                // sample start bit value at mid-point, for start bit counter
                // value = 7 is midpoint
                // wait for rx to transition from 1 to 0
                if(rx == 0 && count == ((NUM_CLKS_PER_BIT-1)/2)) begin
                    done <= 0;
                    state <= RX_DATA_BIT0;
                    count <= 0;
                    dout <= 0;
                end else begin
```

```

count <= count + 1;
end
end
RX_DATA_BIT0: begin
// sample start bit value at mid-point
// for each databit to get midpoint count value is 16
// counting starts from midpoint of previous bit and ends at midpoint
// of current data bit
// Student to fill rest of the code
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT1;
count <= 0;
dout[0] <= rx;
end
else begin
state <= RX_DATA_BIT0;
count <= count + 1;
end
end
// Student to fill rest of the code for all remaining data bits and stop bit
RX_DATA_BIT1: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT2;
count <= 0;
dout[1] <= rx;
end
else begin
state <= RX_DATA_BIT1;
count <= count + 1;
end
end
RX_DATA_BIT2: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT3;
count <= 0;
dout[2] <= rx;
end
else begin
state <= RX_DATA_BIT2;
count <= count + 1;
end
end

```

```

end
RX_DATA_BIT3: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT4;
count <= 0;
dout[3] <= rx;
end
else begin
state <= RX_DATA_BIT3;
count <= count + 1;
end
end
RX_DATA_BIT4: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT5;
count <= 0;
dout[4] <= rx;
end
else begin
state <= RX_DATA_BIT4;
count <= count + 1;
end
end
RX_DATA_BIT5: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT6;
count <= 0;
dout[5] <= rx;
end
else begin
state <= RX_DATA_BIT5;
count <= count + 1;
end
end
RX_DATA_BIT6: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_DATA_BIT7;
count <= 0;
dout[6] <= rx;
end

```

```


else begin
state <= RX_DATA_BIT6;
count <= count + 1;
end
end
RX_DATA_BIT7: begin
if(count == (NUM_CLKS_PER_BIT-1)) begin
done <= 0;
state <= RX_STOP_BIT;
count <= 0;
dout[7] <= rx;
end
else begin
state <= RX_DATA_BIT7;
count <= count + 1;
end
end
RX_STOP_BIT: begin
if(rx == 1 && count == (NUM_CLKS_PER_BIT -1)) begin
done <= 1;
state <= RX_IDLE;
count <= 0;
end
else begin
state <= RX_STOP_BIT;
count <= count + 1;
end
end
endcase
end
end

```


| | Resource | Usage |
|----|--|-----------|
| 1 | Estimated ALUTs Used | 36 |
| 1 | -- Combinational ALUTs | 36 |
| 2 | -- Memory ALUTs | 0 |
| 3 | -- LUT_REGS | 0 |
| 2 | Dedicated logic registers | 24 |
| 3 | | |
| 4 | Estimated ALUTs Unavailable | 14 |
| 1 | -- Due to unpartnered combinational logic | 14 |
| 2 | -- Due to Memory ALUTs | 0 |
| 5 | | |
| 6 | Total combinational functions | 36 |
| 7 | Combinational ALUT usage by number of inputs | |
| 1 | -- 7 input functions | 0 |
| 2 | -- 6 input functions | 14 |
| 3 | -- 5 input functions | 7 |
| 4 | -- 4 input functions | 10 |
| 5 | -- <=3 input functions | 5 |
| 8 | | |
| 9 | Combinational ALUTs by mode | |
| 1 | -- normal mode | 36 |
| 2 | -- extended LUT mode | 0 |
| 3 | -- arithmetic mode | 0 |
| 4 | -- shared arithmetic mode | 0 |
| 10 | | |
| 11 | Estimated ALUT/register pairs used | 50 |
| 12 | | |
| 13 | Total registers | 24 |
| 1 | -- Dedicated logic registers | 24 |
| 2 | -- I/O registers | 0 |
| 3 | -- LUT_REGS | 0 |
| 14 | | |
| 15 | | |
| 16 | I/O pins | 12 |
| 17 | | |
| 18 | DSP block 18-bit elements | 0 |
| 19 | | |
| 20 | Maximum fan-out node | clk~input |
| 21 | Maximum fan-out | 24 |
| 22 | Total fan-out | 252 |

- resource usage
- RTL schematic


| | Resource | Usage |
|----|-----------------|-------|
| 23 | Average fan-out | 3.00 |

 

- Modelsim

 

- FSM Diagram

 

| | Source State | Destination State | Condition |
|----|--------------|-------------------|---|
| 1 | RX_DATA_BIT0 | RX_DATA_BIT0 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 2 | RX_DATA_BIT0 | RX_IDLE | (rstn) |
| 3 | RX_DATA_BIT0 | RX_DATA_BIT1 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 4 | RX_DATA_BIT1 | RX_IDLE | (rstn) |
| 5 | RX_DATA_BIT1 | RX_DATA_BIT1 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 6 | RX_DATA_BIT1 | RX_DATA_BIT2 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 7 | RX_DATA_BIT2 | RX_DATA_BIT3 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 8 | RX_DATA_BIT2 | RX_IDLE | (rstn) |
| 9 | RX_DATA_BIT2 | RX_DATA_BIT2 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 10 | RX_DATA_BIT3 | RX_DATA_BIT3 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 11 | RX_DATA_BIT3 | RX_DATA_BIT4 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 12 | RX_DATA_BIT3 | RX_IDLE | (rstn) |
| 13 | RX_DATA_BIT4 | RX_DATA_BIT4 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 14 | RX_DATA_BIT4 | RX_IDLE | (rstn) |
| 15 | RX_DATA_BIT4 | RX_DATA_BIT5 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 16 | RX_DATA_BIT5 | RX_DATA_BIT6 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 17 | RX_DATA_BIT5 | RX_IDLE | (rstn) |
| 18 | RX_DATA_BIT5 | RX_DATA_BIT5 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 19 | RX_DATA_BIT6 | RX_DATA_BIT6 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 20 | RX_DATA_BIT6 | RX_IDLE | (rstn) |
| 21 | RX_DATA_BIT6 | RX_DATA_BIT7 | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 22 | RX_DATA_BIT7 | RX_STOP_BIT | (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 23 | RX_DATA_BIT7 | RX_IDLE | (rstn) |
| 24 | RX_DATA_BIT7 | RX_DATA_BIT7 | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 25 | RX_IDLE | RX_START_BIT | (rx).(rstn) |
| 26 | RX_IDLE | RX_IDLE | (rx).(rstn) + (rx) |
| 27 | RX_START_BIT | RX_DATA_BIT0 | (count{0}).(count{1}).(count{2}).(count{3}).(rx).(rstn) |
| 28 | RX_START_BIT | RX_START_BIT | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) |
| 29 | RX_START_BIT | RX_IDLE | (rstn) |
| 30 | RX_STOP_BIT | RX_STOP_BIT | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rx).(rstn) |
| 31 | RX_STOP_BIT | RX_IDLE | (count{0}).(rstn) + (count{0}).(count{1}).(rstn) + (count{0}).(count{1}).(count{2}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rstn) + (count{0}).(count{1}).(count{2}).(count{3}).(rx).(rstn) |

testbench

```
# Loading sv_std.std
# Loading work.uart_rx_testbench
# Loading work.uart_rx
add wave -position insertpoint \
sim:/uart_rx_testbench/CLK_PERIOD_NS \
sim:/uart_rx_testbench/NUM_SERIAL_BITS \
sim:/uart_rx_testbench/NUM_CLKS_PER_BIT \
sim:/uart_rx_testbench/BIT_PERIOD_NS \
sim:/uart_rx_testbench/clock \
sim:/uart_rx_testbench/clock_by_n \
sim:/uart_rx_testbench/rstn \
sim:/uart_rx_testbench/rx \
sim:/uart_rx_testbench/done \
sim:/uart_rx_testbench/dout \
sim:/uart_rx_testbench/byte_data
VSI8> run -all
# Test Passed - Correct Byte Received time= 3200 expected=a5 actual=a5
# Test Passed - Correct Byte Received time= 6400 expected=a8 actual=a8
# Test Passed - Correct Byte Received time= 9600 expected=ab actual=ab
# Test Passed - Correct Byte Received time= 12800 expected=ae actual=ae
```


- Uart Tx-Rx Code

```
// UART TX RTL Code
module uart_top #(parameter NUM_CLKS_PER_BIT=16)
(input logic tx_clk, tx_rstn, rx_clk, rx_rstn,
input logic[7:0] tx_din,
input logic tx_start,
output logic tx_done, rx_done,
output logic[7:0] rx_dout);
// wire to connect output of uart_tx "tx" signal to
// uart_rx "rx" signal
logic serial_data_bit;
// Instantiate uart transmitter module
// student to add code
uart_tx #(.NUM_CLKS_PER_BIT(NUM_CLKS_PER_BIT)) inst1(
.clk(tx_clk),
.rstn(tx_rstn),
.din(tx_din),
.start(tx_start),
.done(tx_done),
.tx(serial_data_bit)
);
// Instantiate uart receiver module
// student to add code
uart_rx #(.NUM_CLKS_PER_BIT(NUM_CLKS_PER_BIT)) inst2(
.clk(rx_clk),
.rstn(rx_rstn),
.rx(serial_data_bit),
.done(rx_done),
.dout(rx_dout)
);
endmodule: uart_top
```



| | Resource | Usage |
|----|--|--------------|
| 1 | Estimated ALUTs Used | 56 |
| 1 | -- Combinational ALUTs | 56 |
| 2 | -- Memory ALUTs | 0 |
| 3 | -- LUT_REGS | 0 |
| 2 | Dedicated logic registers | 38 |
| 3 | | |
| 4 | Estimated ALUTs Unavailable | 22 |
| 1 | -- Due to unpartnered combinational logic | 22 |
| 2 | -- Due to Memory ALUTs | 0 |
| 5 | | |
| 6 | Total combinational functions | 56 |
| 7 | Combinational ALUT usage by number of inputs | |
| 1 | -- 7 input functions | 2 |
| 2 | -- 6 input functions | 20 |
| 3 | -- 5 input functions | 13 |
| 4 | -- 4 input functions | 14 |
| 5 | -- <=3 input functions | 7 |
| 8 | | |
| 9 | Combinational ALUTs by mode | |
| 1 | -- normal mode | 54 |
| 2 | -- extended LUT mode | 2 |
| 3 | -- arithmetic mode | 0 |
| 4 | -- shared arithmetic mode | 0 |
| 10 | | |
| 11 | Estimated ALUT/register pairs used | 78 |
| 12 | | |
| 13 | Total registers | 38 |
| 1 | -- Dedicated logic registers | 38 |
| 2 | -- I/O registers | 0 |
| 3 | -- LUT_REGS | 0 |
| 14 | | |
| 15 | | |
| 16 | I/O pins | 23 |
| 17 | | |
| 18 | DSP block 18-bit elements | 0 |
| 19 | | |
| 20 | Maximum fan-out node | rx_clk~input |
| 21 | Maximum fan-out | 24 |
| 22 | Total fan-out | 397 |

| | Resource | Usage |
|----|-----------------|-------|
| 23 | Average fan-out | 2.84 |


- Resource Usage
- RTL Schematic

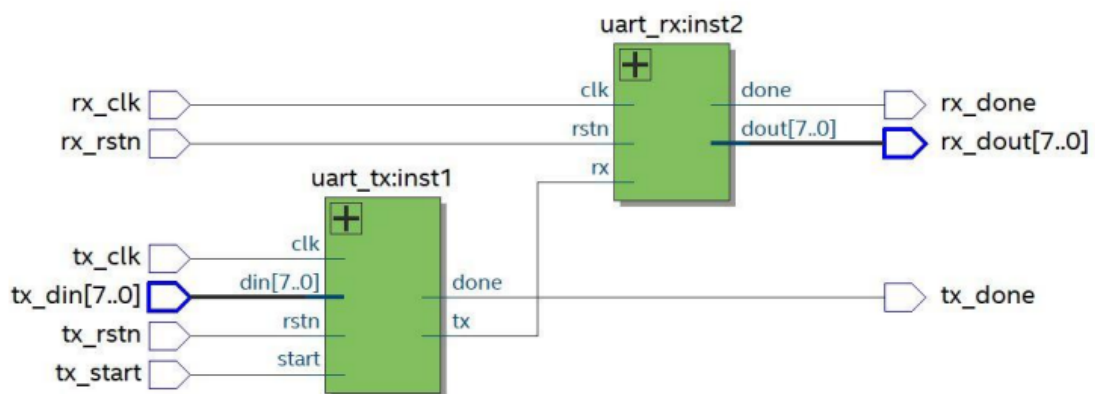 

- Waveform



- FSM Diagram

 

| | Source State | Destination State | Condition |
|----|--------------|-------------------|--|
| 1 | RX_DATA_BIT0 | RX_DATA_BIT0 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 2 | RX_DATA_BIT0 | RX_DATA_BIT1 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 3 | RX_DATA_BIT0 | RX_IDLE | $\{rstn\}$ |
| 4 | RX_DATA_BIT1 | RX_DATA_BIT2 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 5 | RX_DATA_BIT1 | RX_DATA_BIT1 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 6 | RX_DATA_BIT1 | RX_IDLE | $\{rstn\}$ |
| 7 | RX_DATA_BIT2 | RX_DATA_BIT2 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 8 | RX_DATA_BIT2 | RX_IDLE | $\{rstn\}$ |
| 9 | RX_DATA_BIT2 | RX_DATA_BIT3 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 10 | RX_DATA_BIT3 | RX_DATA_BIT4 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 11 | RX_DATA_BIT3 | RX_IDLE | $\{rstn\}$ |
| 12 | RX_DATA_BIT3 | RX_DATA_BIT3 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 13 | RX_DATA_BIT4 | RX_DATA_BIT4 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 14 | RX_DATA_BIT4 | RX_IDLE | $\{rstn\}$ |
| 15 | RX_DATA_BIT4 | RX_DATA_BIT5 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 16 | RX_DATA_BIT5 | RX_IDLE | $\{rstn\}$ |
| 17 | RX_DATA_BIT5 | RX_DATA_BIT6 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 18 | RX_DATA_BIT5 | RX_DATA_BIT5 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 19 | RX_DATA_BIT6 | RX_IDLE | $\{rstn\}$ |
| 20 | RX_DATA_BIT6 | RX_DATA_BIT6 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 21 | RX_DATA_BIT6 | RX_DATA_BIT7 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 22 | RX_DATA_BIT7 | RX_IDLE | $\{rstn\}$ |
| 23 | RX_DATA_BIT7 | RX_STOP_BIT | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 24 | RX_DATA_BIT7 | RX_DATA_BIT7 | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 25 | RX_IDLE | RX_IDLE | $\{rx\}, \{rstn\} + \{rx\}$ |
| 26 | RX_IDLE | RX_START_BIT | $\{rx\}, \{rstn\}$ |
| 27 | RX_START_BIT | RX_DATA_BIT0 | $\{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rx\}, \{rstn\}$ |
| 28 | RX_START_BIT | RX_IDLE | $\{rstn\}$ |
| 29 | RX_START_BIT | RX_START_BIT | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rx\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rstn\}$ |
| 30 | RX_STOP_BIT | RX_IDLE | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rx\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rx\}$ |
| 31 | RX_STOP_BIT | RX_STOP_BIT | $\{count[0]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rx\}, \{rstn\} + \{count[0]\}, \{count[1]\}, \{count[2]\}, \{count[3]\}, \{rx\}, \{rstn\}$ |

```

# Loading sv_std.std
# Loading work.uart_top_testbench
# Loading work.uart_top
# Loading work.uart_tx
# Loading work.uart_rx
add wave -position insertpoint \
sim:/uart_top_testbench/CLK_PERIOD_NS \
sim:/uart_top_testbench/NUM_SERIAL_BITS \
sim:/uart_top_testbench/NUM_CLKS_PER_BIT \
sim:/uart_top_testbench/TRANSMIT_TIME \
sim:/uart_top_testbench/clock \
sim:/uart_top_testbench/clock_by_n \
sim:/uart_top_testbench/rstn \
sim:/uart_top_testbench/start \
sim:/uart_top_testbench/done \
sim:/uart_top_testbench/ready \
sim:/uart_top_testbench/din \
sim:/uart_top_testbench/dout \
sim:/uart_top_testbench/byte_data \
sim:/uart_top_testbench/index
VSI6> run -all
# Test Passed - Correct Byte Received time= 3070 expected=a5 actual=a5
# Test Passed - Correct Byte Received time= 6430 expected=a8 actual=a8
# Test Passed - Correct Byte Received time= 9710 expected=ab actual=ab
# Test Passed - Correct Byte Received time= 12990 expected=ae actual=ae

```

- Transcript